$$t = 0$$

$$R = 500 \Omega$$

$$L = 0.5 \text{ H}$$

$$C = 4 \mu \text{F}$$

$$u_C(t)$$

$$u(t) = \sqrt{2} \cdot 220 \cos(100\pi t) \text{ V}$$